

TUTORIAL 3

LOGIC GATES


PDS0101: INTRODUCTION TO DIGITAL SYSTEMS
TRI 2, 2022-2023



QUESTION 1

Draw the LOGIC SYMBOL and construct the TRUTH TABLES and TIMING DIAGRAM for the following gates showing all possible input combinations


LOGIC SYMBOL
1-input inverter

 

$$2^n \xleftarrow{\text{input}} = 2' = \underline{\underline{2}} < \begin{matrix} 1 \\ 0 \end{matrix}$$

TRUTH TABLES


| INPUT | OUTPUT | |
|-------|-----------|----|
| A | \bar{A} | A' |
| 0 | 1 | |
| 1 | 0 | |

 

TIMING DIAGRAM

inverter
NOT

only ONE input

 

AND

OR

NAND

NOR


XOR

XNOR



negative AND

negative OR

at least two input

 

Input AND output

  


QUESTION 2

Draw the LOGIC SYMBOL and construct the TRUTH TABLES and TIMING DIAGRAM for the following gates showing all possible input combinations

LOGIC SYMBOL

4-input (quad input) AND gate

 


$$2^n = 2^4 = 16 \text{ possible input combinations}$$

Example: 0010, 1101, 0001

| INPUT | | | | OUTPUT |
|-------|---|---|---|----------|
| A | B | C | D | X = ABCD |
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 0 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 0 | 0 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 | 1 |

4-input (quad input)AND gate

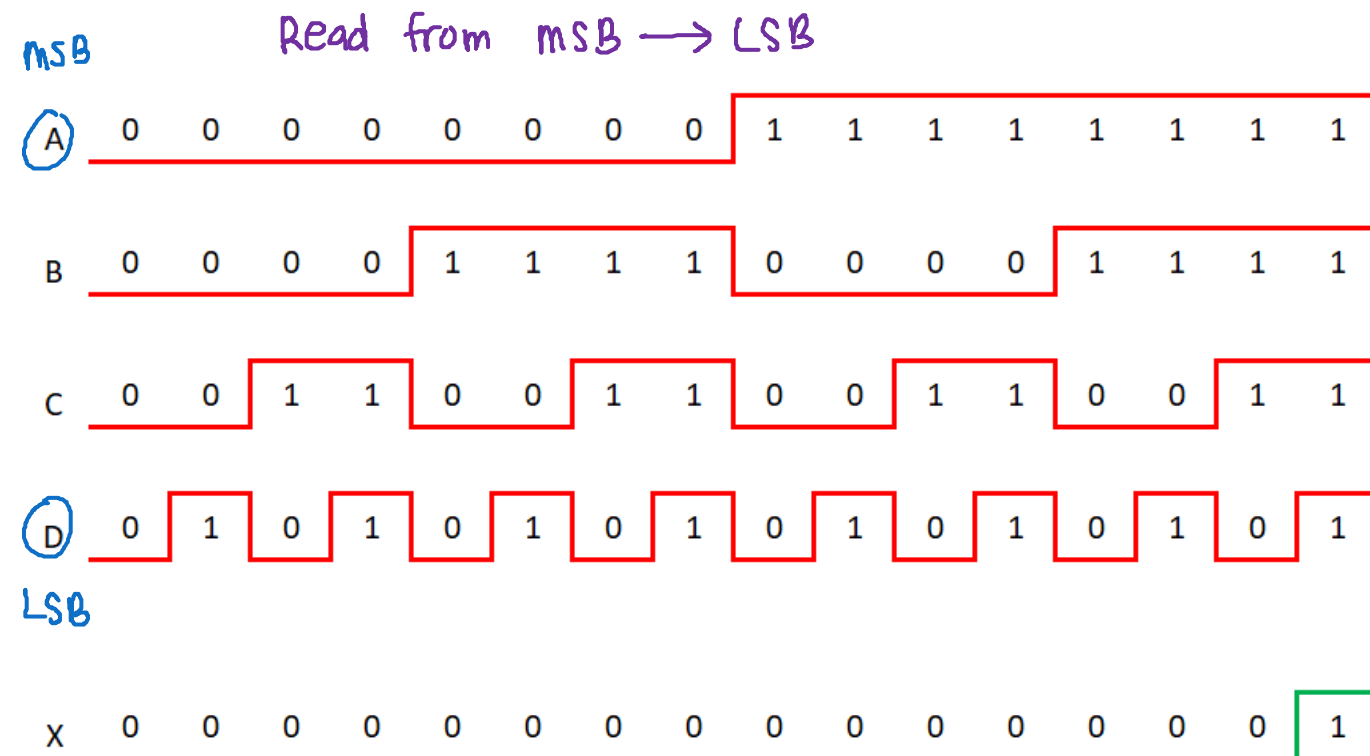

TIMING DIAGRAM

if ALL input ONE ;
output = ONE

6 input AND gate

| Input | Output |
|---------|--------|
| 111 111 | → 1 |
| 111 101 | → 0 |
| 011 111 | → 0 |


7 input AND gate

| input | output |
|----------|--------|
| 111 1111 | → 1 |

QUESTION 3

Draw the LOGIC SYMBOL and construct the TRUTH TABLES and TIMING DIAGRAM for the following gates showing all possible input combinations

LOGIC SYMBOL
4-input OR gate

 


$$2^n = 2^4 = 16 \text{ possible input combinations}$$

Example : 0010, 0011, 1110,
Input 1111, 1010, 0000 ...

| TRUTH TABLES | | INPUT | | OUTPUT | |
|--------------|---|-------|---|-------------|--|
| A | B | C | D | X = A+B+C+D | |
| 0 | 0 | 0 | 0 | 0 | |
| 0 | 0 | 0 | 1 | 1 | |
| 0 | 0 | 1 | 0 | 1 | |
| 0 | 0 | 1 | 1 | 1 | |
| 0 | 1 | 0 | 0 | 1 | |
| 0 | 1 | 0 | 1 | 1 | |
| 0 | 1 | 1 | 0 | 1 | |
| 0 | 1 | 1 | 1 | 1 | |
| 1 | 0 | 0 | 0 | 1 | |
| 1 | 0 | 0 | 1 | 1 | |
| 1 | 0 | 1 | 0 | 1 | |
| 1 | 0 | 1 | 1 | 1 | |
| 1 | 1 | 0 | 0 | 1 | |
| 1 | 1 | 0 | 1 | 1 | |
| 1 | 1 | 1 | 0 | 1 | |
| 1 | 1 | 1 | 1 | 1 | |

4-input OR gate

 

TIMING DIAGRAM

If ALL input ZERO ;
 outp ut = ZERO



QUESTION 4

Draw the LOGIC SYMBOL and construct the TRUTH TABLES and TIMING DIAGRAM for the following gates showing all possible input combinations

LOGIC SYMBOL

4-input NAND gate


input (NOT AND)

  

$$2^n = 2^4 = 16 \text{ possible input combinations}$$

| TRUTH TABLES | | INPUT | | OUTPUT |
|--------------|---|-------|---|---------------|
| A | B | C | D | $X = (ABCD)'$ |
| 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 0 | 1 | 1 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 0 | 1 | 1 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 1 | 1 |
| 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 0 | 1 | 1 |
| 1 | 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 | 0 |

4-input NAND gate

 

TIMING DIAGRAM

AND

If All input ONE, output ONE

NAND (Not And)

If All input ONE, output ZERO


invert

QUESTION 5

Draw the LOGIC SYMBOL and construct the TRUTH TABLES and TIMING DIAGRAM for the following gates showing all possible input combinations

LOGIC SYMBOL


4-input NOR gate
(NOT OR)

 

2^n ← input
 $= 2^4 = 16$ possible Input Combination

| TRUTH TABLES | | INPUT | | OUTPUT |
|--------------|---|-------|---|--------------------------|
| A | B | C | D | $X = \overline{A+B+C+D}$ |
| 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 0 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 0 | 0 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 | 0 |

4-input NOR gate

 

TIMING DIAGRAM

OR ($A+B+C+D$)
 if ALL input ZERO, output ZERO


NOR ($\overline{A+B+C+D}$)
 if ALL input ZERO; output ONE ↙ invert

QUESTION 6

Draw the LOGIC SYMBOL and construct the TRUTH TABLES for the following gates showing all possible input combinations

LOGIC SYMBOL

3-input XOR gate

 

$2^3 = 8$ possible input combinations

total number of input high (one)
is ODD number ;
then output ONE






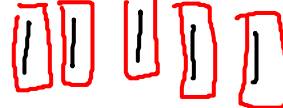
TRUTH TABLES

| INPUT | | | OUTPUT |
|-------|---|---|---------------------------|
| A | B | C | $W = A \oplus B \oplus C$ |
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 |


XOR gate

1, 3, 5, 7, ...

total number of input high (ONE) is ODD number, then output = ONE

| Example <u>input</u> | | total number of input high | <u>XOR</u> <u>output</u> | <u>XNOR</u> |
|----------------------|---|----------------------------|-----------------------------|-------------|
| a) |  | 3 input high | 1 | 0 |
| b) |  | 1 input high | 1 | 0 |
| c) |  | 2 input high | 0 | 1 |
| d) |  | 1 input high | 1 | 0 |
| e) |  | 2 input high | 0 | 1 |
| f) |  | 5 input high | 1 | 0 |


TIMING DIAGRAM

 

QUESTION 7

Draw the LOGIC SYMBOL and construct the TRUTH TABLES for the following gates showing all possible input combinations

LOGIC SYMBOL
3-input XNOR gate

 

$2^n = 2^3 = 8$ possible input combinations

$$W = A \oplus B \oplus C$$

$$\bar{W} = \overline{A \oplus B \oplus C}$$


TRUTH TABLES

| INPUT | | | xOR | OUTPUT | xNOR |
|-------|---|---|---------------------------|------------------------------------|------|
| A | B | C | $W = A \oplus B \oplus C$ | $\bar{W} = (A \oplus B \oplus C)'$ | |
| 0 | 0 | 0 | 0 | | 1 |
| 0 | 0 | 1 | 1 | | 0 |
| 0 | 1 | 0 | 1 | | 0 |
| 0 | 1 | 1 | 0 | | 1 |
| 1 | 0 | 0 | 1 | | 0 |
| 1 | 0 | 1 | 0 | | 1 |
| 1 | 1 | 0 | 0 | | 1 |
| 1 | 1 | 1 | 1 | | 0 |

QUESTION 10

Draw the LOGIC SYMBOL and construct the TRUTH TABLES for the following gates showing all possible input combinations

LOGIC SYMBOL
3-input negative-AND gate

 

$2^3 = 8$ possible input combinations

If ALL input ONE, output = ONE

\overline{ABC} X


TRUTH TABLES $\bar{A}\bar{B}\bar{C}$

| INPUT | | | | | | OUTPUT |
|-------|---|---|----|----|----|--------|
| A | B | C | A' | B' | C' | A'B'C' |
| 0 | 0 | 0 | 1 | 1 | 1 | 1 |
| 0 | 0 | 1 | 1 | 1 | 0 | 0 |
| 0 | 1 | 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 1 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 | 1 | 0 |
| 1 | 1 | 1 | 0 | 0 | 0 | 0 |

Invert Invert Invert

negative AND gate

$\bar{A} \bar{B} \bar{C}$

 


\neq

NOT AND gate
(NAND)

\neq

\overline{ABC}

\neq

 

DeMorgan

negative AND gate = NOR gate
(NOT OR)

$$\bar{A}\bar{B}\bar{C}\bar{D}$$

$$= \overline{A+B+C+D}$$

QUESTION 10

3-input negative-AND gate equivalent with 3-input NOR gate

3-input negative-AND gate

TRUTH TABLES

$$\overline{A}\overline{B}\overline{C}$$

=

$$\overline{A+B+C}$$

| INPUT | | | OUTPUT | | | |
|-------|---|---|--------|----|----|--------|
| A | B | C | A' | B' | C' | A'B'C' |
| 0 | 0 | 0 | 1 | 1 | 1 | 1 |
| 0 | 0 | 1 | 1 | 1 | 0 | 0 |
| 0 | 1 | 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 1 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 | 1 | 0 |
| 1 | 1 | 1 | 0 | 0 | 0 | 0 |


(NOT OR)
3-input NOR gate

TRUTH TABLES

| INPUT | | | OR | OUTPUT NOR |
|-------|---|---|-------|------------|
| A | B | C | A+B+C | (A+B+C)' |
| 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 | 0 |

 QUESTION 11

Draw the LOGIC SYMBOL and construct the TRUTH TABLES for the following gates showing all possible input combinations



TRUTH TABLES

| INPUT | | | | | | OUTPUT |
|-------|---|---|----|----|----|----------|
| A | B | C | A' | B' | C' | A'+B'+C' |
| 0 | 0 | 0 | 1 | 1 | 1 | 1 |
| 0 | 0 | 1 | 1 | 1 | 0 | 1 |
| 0 | 1 | 0 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 1 | 0 | 0 | 1 |
| 1 | 0 | 0 | 0 | 1 | 1 | 1 |
| 1 | 0 | 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 0 | 0 | 1 | 1 |
| 1 | 1 | 1 | 0 | 0 | 0 | 0 |

QUESTION 11

3-input negative-OR gate equivalent with 3-input NAND gate

3-input negative-OR gate

TRUTH TABLES

$$\bar{A} + \bar{B} + \bar{C} = \overline{ABC}$$

| INPUT | | | OUTPUT | | | |
|-------|---|---|--------|----|----|----------|
| A | B | C | A' | B' | C' | A'+B'+C' |
| 0 | 0 | 0 | 1 | 1 | 1 | 1 |
| 0 | 0 | 1 | 1 | 1 | 0 | 1 |
| 0 | 1 | 0 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 1 | 0 | 0 | 1 |
| 1 | 0 | 0 | 0 | 1 | 1 | 1 |
| 1 | 0 | 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 0 | 0 | 1 | 1 |
| 1 | 1 | 1 | 0 | 0 | 0 | 0 |

3-input NAND gate

TRUTH TABLES

| INPUT | | | OUTPUT | |
|-------|---|---|--------|--------|
| A | B | C | ABC | (ABC)' |
| 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 0 |



negative OR gate = NOT AND (NAND) gate

$$\bar{A} + \bar{B} + \bar{C} + \bar{D} = \overline{ABCD}$$

APPLIED KNOWLEDGE QUESTIONS 1


A series of cascaded inverters is shown in the figure below. Determine the logic level outputs at B, C, D and F if the V_{IN} signal at A is given as shown.

$$\bar{\bar{A}} = A$$

 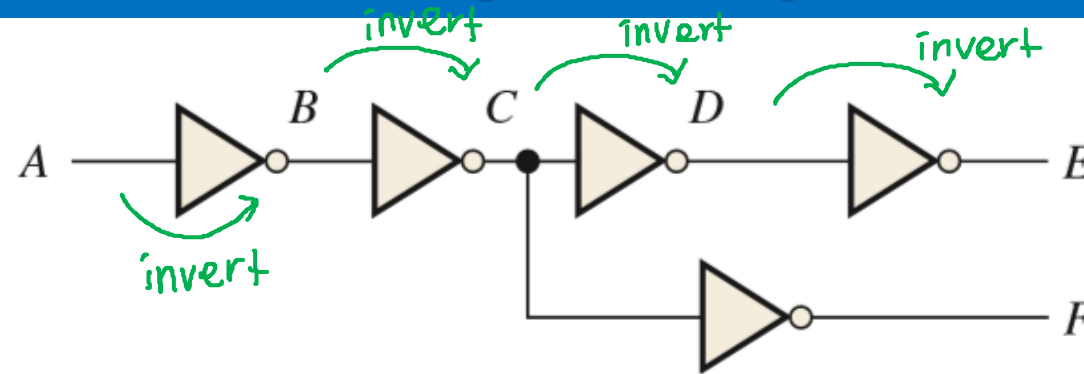


APPLIED KNOWLEDGE QUESTIONS 2 (i)

 Determine the individual outputs of X to the tri-input gates below based on the timing diagrams shown for inputs A, B and C



If ALL input ONE, output = ONE

timing diagram

 


APPLIED KNOWLEDGE QUESTIONS 2 (ii)

Determine the individual outputs of X to the tri-input gates below based on the timing diagrams shown for inputs A, B and C




 AND if All input ONE, output ONE ↓ invert
NAND if All input ONE, output ZERO




APPLIED KNOWLEDGE QUESTIONS 2 (iii)

 Determine the individual outputs of X to the tri-input gates below based on the timing diagrams shown for inputs A, B and C






 OR
 IF All Input ZERO, output ZERO ↓ invert
 NOR (NOT OR)
 IF All input ZERO, output ONE



   QUESTION 3 (i and ii)



Determine the individual outputs of X / Y to the quad-input gates below based on the timing diagrams shown for inputs A, B, C and D



| INPUT | | | | OUTPUT | |
|-------|---|---|---|----------|--------|
| A | B | C | D | X = ABCD | Y = X' |
| 0 | 0 | 0 | 0 | 0 | 1 |
| 1 | 0 | 0 | 0 | 0 | 1 |
| 1 | 1 | 0 | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 | 0 |
| 0 | 1 | 1 | 1 | 0 | 1 |
| 0 | 0 | 1 | 1 | 0 | 1 |
| 0 | 0 | 0 | 1 | 0 | 1 |
| 0 | 0 | 0 | 0 | 0 | 1 |

  QUESTION 3 (iii)


Determine the individual outputs of X / Y to the quad-input gates below based on the timing diagrams shown for inputs A, B, C and D




| INPUT | | | | XOR | OUTPUT | XNOR |
|-------|---|---|---|------------------------------------|----------|------|
| A | B | C | D | $Y = A \oplus B \oplus C \oplus D$ | $X = Y'$ | |
| 0 | 0 | 0 | 0 | 0 | | 1 |
| 1 | 0 | 0 | 0 | 1 | | 0 |
| 1 | 1 | 0 | 0 | 0 | | 1 |
| 1 | 1 | 1 | 0 | 1 | | 0 |
| 1 | 1 | 1 | 1 | 0 | | 1 |
| 0 | 1 | 1 | 1 | 1 | | 0 |
| 0 | 0 | 1 | 1 | 0 | | 1 |
| 0 | 0 | 0 | 1 | 1 | | 0 |
| 0 | 0 | 0 | 0 | 0 | | 1 |

 QUESTION 4

Complete the timing diagram for the two gates below based on the inputs A and B shown. What conclusions can you derive from the output of the gates?



| INPUT | | OUTPUT | |
|-------|---|-------------|---------------|
| A | B | $X = (AB)'$ | $X = A' + B'$ |
| 0 | 0 | 1 | 1 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 |

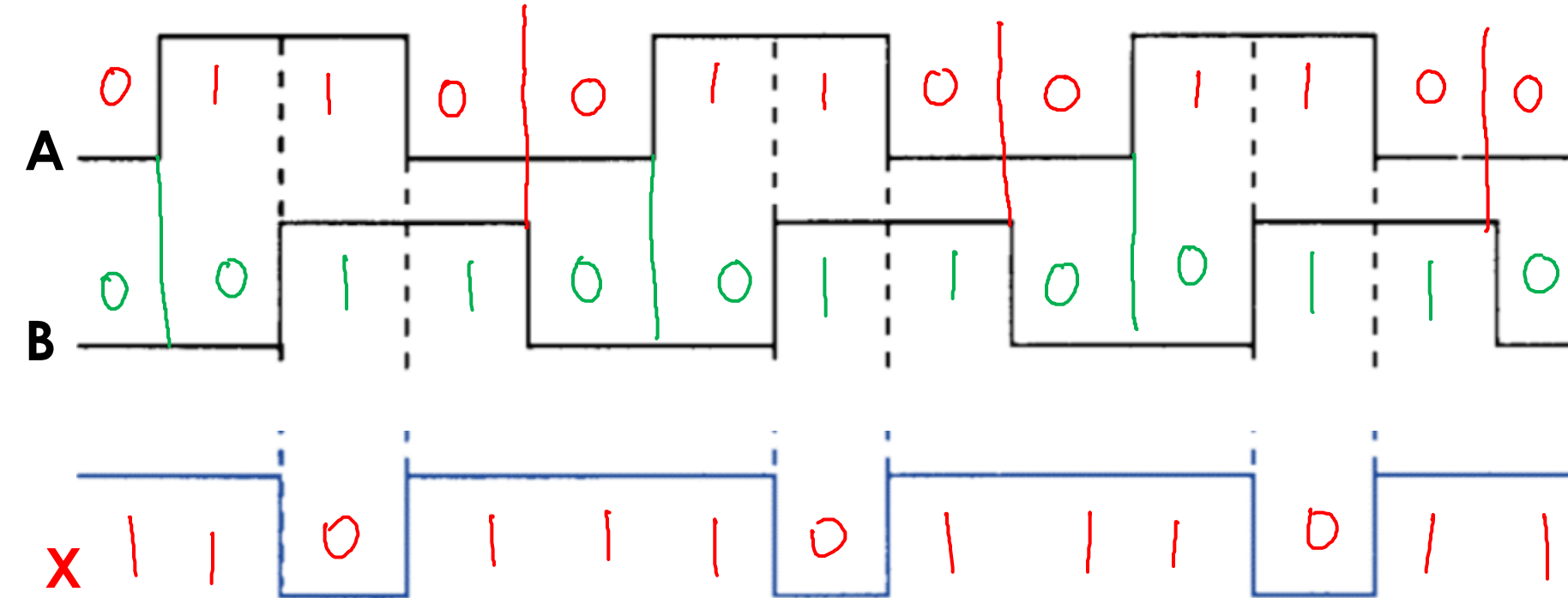

Conclusion :

input $\begin{matrix} A \\ B \end{matrix}$


$2^n = 2^2 = 4$ possible input combinations

| | | NAND gate | | negative OR | | |
|---|---|-----------|-----------------|----------------|----------------|-------------------------------|
| A | B | AB | \overline{AB} | \overline{A} | \overline{B} | $\overline{A} + \overline{B}$ |
| 0 | 0 | 0 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 1 | 0 | 1 | 1 |
| 1 | 1 | 1 | 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | 1 | 0 | 1 |

$\overline{AB} = \overline{A} + \overline{B}$

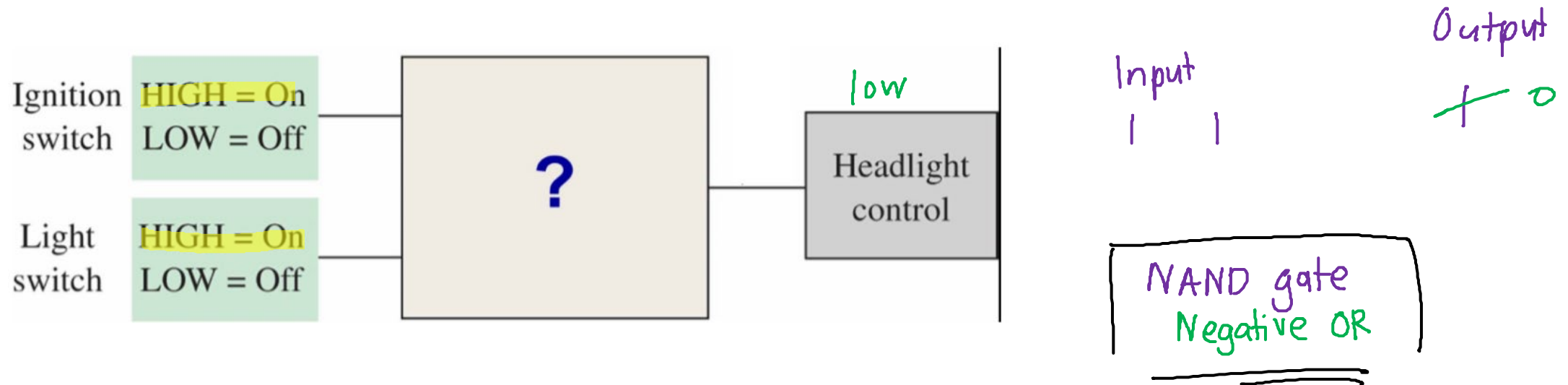QUESTION 5

The headlights of a car only turn on (light up) when the car's ignition is turned ON with the key and the headlight switch is turned ON. Assuming that the headlight requires a LOW signal to turn it ON, what gate would be suitable to fit in the blank below to complete the circuit? Explain your answer.



Both inputs need to be **high (ON)** to activate its output. (**AND gate**)
The headlight is activated upon a **LOW signal**, inverse of the output.
Hence the **NAND gate** is used. (optional **negative-OR**)

END DISCUSSIONS

ANY QUESTIONS ??

