

TUTORIAL 6

FUNCTIONS OF COMBINATIONAL LOGIC

PDS0101: INTRODUCTION TO DIGITAL SYSTEMS
TRI 2, 2022-2023



QUESTION 1 : Perform the following to construct a HALF-ADDER logic circuit

a) Complete the **TRUTH TABLE** for **1-bit BINARY ADDITION**

$2^2 = 4$ possible input combinations

← input → ← output →

Augend(A)	Addend(B)	Carry Out	Sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$\begin{array}{r} 0 \\ + 0 \\ \hline 0 \end{array}$$

$$\begin{array}{r} 0 \\ + 1 \\ \hline 1 \end{array}$$

$$\begin{array}{r} 1 \\ + 0 \\ \hline 1 \end{array}$$

$$\begin{array}{r} 1 \\ + 1 \\ \hline 10 \end{array}$$

decimal 2

↑ ↑
Cout sum

b) Derive the Boolean expressions (SOP) for **SUM** and **CARRY OUT**


$$C_{out} = AB \qquad Sum = A \oplus B / A\bar{B} + \bar{A}B$$

QUESTION 1 : Perform the following to construct a HALF-ADDER logic circuit

c) Combine the sum and carry out expressions and **draw** the final **logic circuit** for a **half-adder** using only **AND**, **OR** and **NOT** gates



~~$A \oplus B$~~

$$\bar{A}B + A\bar{B} = \text{Sum}$$

 

QUESTION 1 : Perform the following to construct a HALF-ADDER logic circuit

  
d) Draw the **block diagram** for the **half-adder**



Draw parallel adder for $10011 + 11011$ using full adder
(block diagram/logic diagram) \rightarrow 5 bit

MSB LSB
Binary number
A : 10011
B : 11011

$A_5 A_4 A_3 A_2 A_1$

 


Draw parallel adder for $10011 + 11011$ using full adder
 (block diagram/logic diagram) 5 bit

Binary number

A : 10011

B : 11011

101110

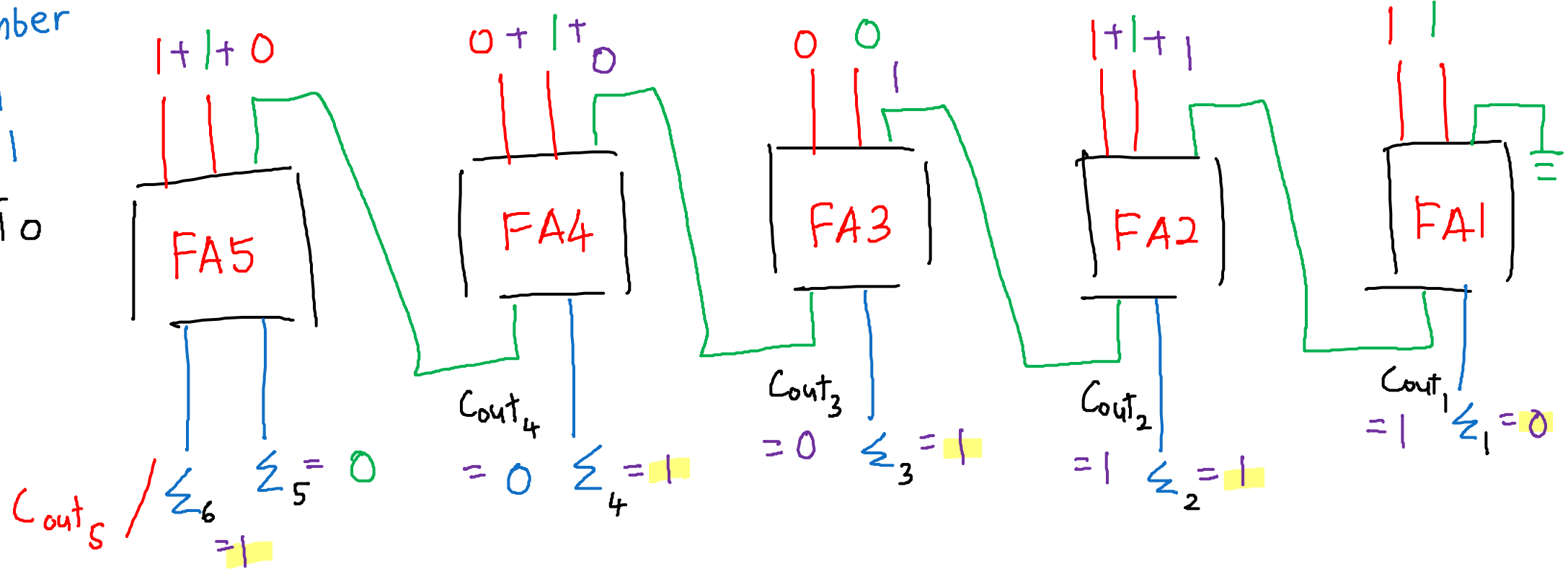

$$\Sigma_6 \Sigma_5 \Sigma_4 \Sigma_3 \Sigma_2 \Sigma_1 = 101110 \quad \text{X}$$


Draw parallel adder for $10011 + 11011$ using full adder and half adder
(block diagram/logic diagram) \rightarrow 5 bit

Binary number

A : 10011

B : 11011


$A_5 A_4 A_3 A_2 A_1$

 

QUESTION 3

Determine the output value for C_{out} and Σ (sum) of a **FULL ADDER**, if the inputs are as shown below

	A	B	C_{in}	C_{out}	Σ (sum)
(a)	1	0	0	0	1
(b)	0	0	1	0	1
(c)	0	1	1	1	0
(d)	1	1	1	1	1

 

QUESTION 4

Determine the possible **FULL ADDER INPUTS** that will produce the following outputs


← output →

	C_{out}	Σ (sum)	A	B	C_{in}
(a)	0	1 	0	1	0
			0	0	1
			1	0	0
(b)	0	0	0	0	0
(c)	1	1	1	1	1
(d)	1	0	1	1	0
			0	1	1
			1	0	1

 QUESTION 5 (a)

For the **PARALLEL ADDERS** below, determine the complete **SUM BY ANALYSIS** of the logical operation of the circuit

$$\begin{array}{r}
 A : 111 \\
 B : 101 \\
 \hline
 1100 \quad \#
 \end{array}$$




$$\Sigma_4 \Sigma_3 \Sigma_2 \Sigma_1 = 1100 \quad \#$$

QUESTION 5 (b)

For the **PARALLEL ADDERS** below, determine the complete **SUM BY ANALYSIS** of the logical operation of the circuit

A : 10101


B : 00111

 

11100

 QUESTION 7


Design a **3-bit parallel adder** by using **full adders**



Draw parallel adder for $A_{16} + 14_8$ using full adder and half adder
(LSB)





$$A_{16} = 1010$$

$$14_8 = 1100$$

 

    QUESTION 8


When a **HIGH output** is detected on the output of the following **decoder circuits**, what is the **binary code signal** appearing on the **INPUTS** assuming that A_0 is LSB?



Decoder

simple decoder/
basic decoder


a) Active High Output

 

b) Active Low Output



decoder that
accept multiple combo
(SOP)

 

line decoder

$n - to - x$

2 - to - 4 line decoder


3 - to - 8 line decoder

4 to 16 line decoder


QUESTION 9

Show the **decoding logic** for the following **codes** if an **active-HIGH** output is required

a) 1101

 


b) 11011

 

QUESTION 9

Show the **decoding logic** for the following **codes** if an **active-HIGH** output is required


c) 101010

 

QUESTION 9

Show the **decoding logic** for the following **codes** if an **active-HIGH** output is required


d) 1110110

 

QUESTION 10

Show the **decoding logic** for the following **codes** if an **active-LOW** output is required


a) 1000

 

QUESTION 10

Show the **decoding logic** for the following **codes** if an **active-LOW** output is required


b) 11100

 

QUESTION 10

Show the **decoding logic** for the following **codes** if an **active-LOW** output is required


c) 111110

 

QUESTION 10


Show the **decoding logic** for the following **codes** if an **active-LOW** output is required

d) 000101

 

QUESTION 11

Design a decoder that detects the presence of the input binary codes of 1010, 1100, 0001 and 1011. The active-HIGH output is required when the correct input is detected.

 

QUESTION 12


Design a **2-to-4-Line Decoder** (with **Enable input**) and **Active LOW** output.
Provide the circuit and truth table.

Handwritten notes:
 - "input" points to the "2" in "2-to-4-Line".
 - "Combination" points to the "4" in "2-to-4-Line".
 - "EN = 0 ; active" points to the "Enable input".
 - "Output = 0" points to the "Active LOW" output.

EN	A	B	D ₀	D ₁	D ₂	D ₃
1	X	X	1	1	1	1
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0

QUESTION 12

Design a **2-to-4-Line Decoder** (with **Enable input**) and **Active LOW** output. Provide the circuit and truth table.

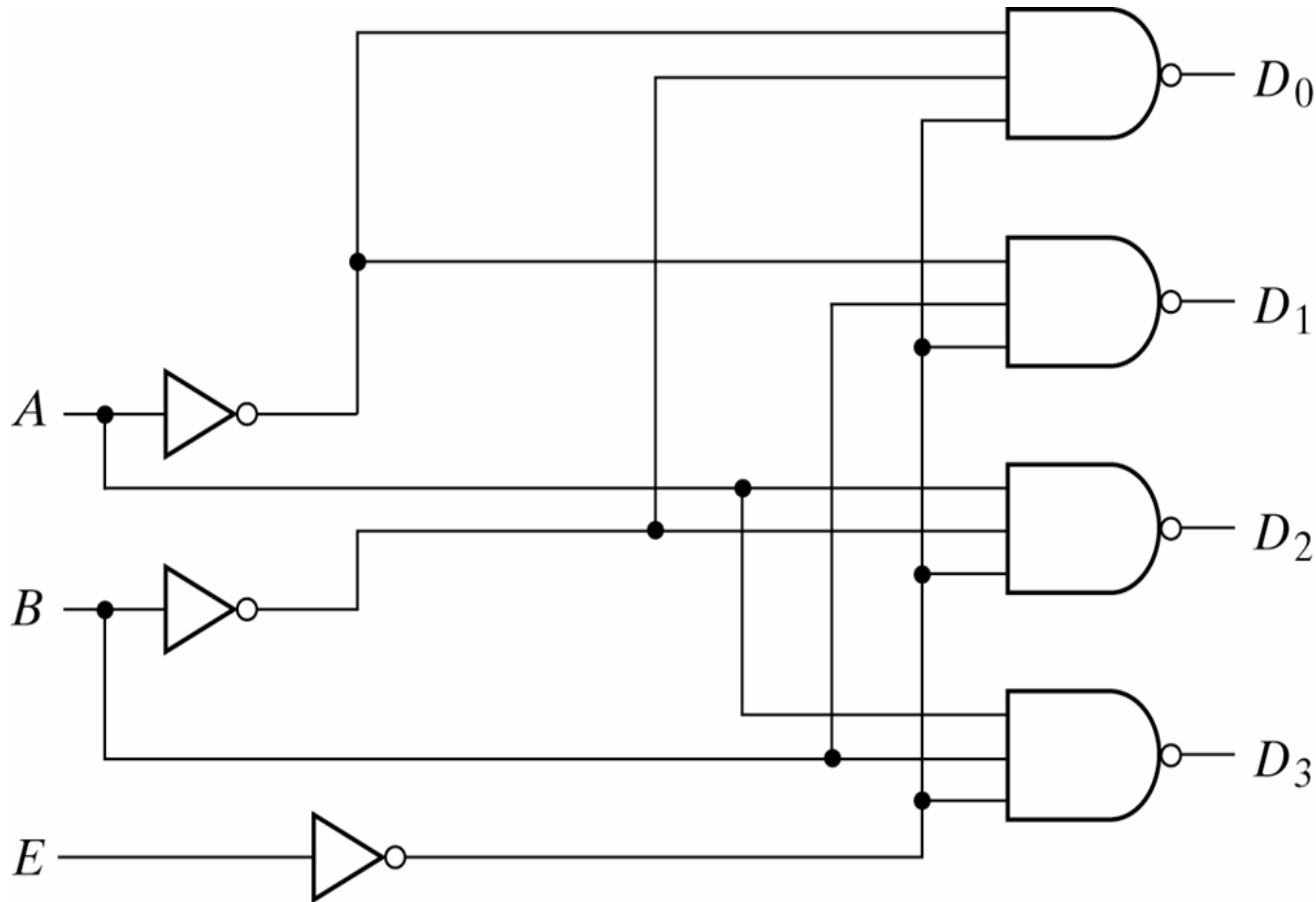

QUESTION 12

Design a **3-to-8-Line Decoder** (with **Enable input**) and **Active HIGH** output.
Provide the circuit and truth table.

EN = 1

Output = 1

EN	A	B	C	D ₀	D ₁	D ₂	D ₃	D ₄	D ₅	D ₆	D ₇
0	X	X	X	0	0	0	0	0	0	0	0
1	0	0	0	1	0	0	0	0	0	0	0
1	0	0	1	0	1	0	0	0	0	0	0
1	0	1	0	0	0	1	0	0	0	0	0
1	0	1	1	0	0	0	1	0	0	0	0
1	1	0	0	0	0	0	0	1	0	0	0
1	1	0	1	0	0	0	0	0	1	0	0
1	1	1	0	0	0	0	0	0	0	1	0
1	1	1	1	0	0	0	0	0	0	0	1

**END DISCUSSIONS
ANY QUESTIONS ??**

