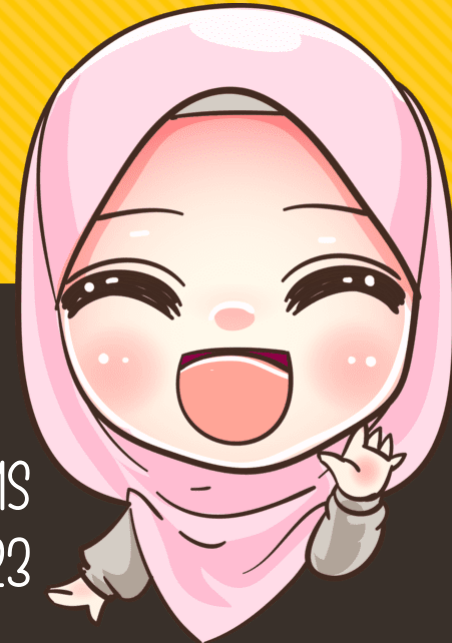


TUTORIAL 4

BOOLEAN ALGEBRA AND LOGIC SIMPLIFICATION

PDS0101: INTRODUCTION TO DIGITAL SYSTEMS
TRI 2, 2022-2023



BASIC RULES OF BOOLEAN ALGEBRA

$$1. A + 0 = A$$

$$2. A + 1 = 1$$

$$3. A \cdot 0 = 0$$

$$4. A \cdot 1 = A$$

$$5. A + A = A$$

$$6. A + \bar{A} = 1$$

$$7. A \cdot A = A$$

$$8. A \cdot \bar{A} = 0$$

$$9. \bar{\bar{A}} = A$$

$$10. A + AB = A$$

$$11. A + \bar{A}B = A + B$$

$$\bar{A} + AB = \bar{A} + B$$


$$12. (A + B)(A + C) = A + BC$$

$$13. \overline{AB} = \bar{A} + \bar{B} \quad \left. \vphantom{\overline{AB}} \right\} \text{DMT}$$

$$14. \overline{A+B} = \bar{A}\bar{B}$$

BASIC RULES OF BOOLEAN ALGEBRA

$$\overline{\overline{A}} = A$$

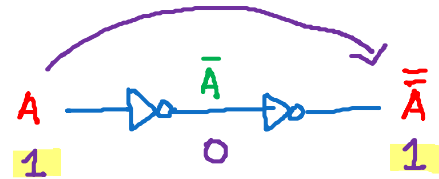

$$2^1 = 2 < \begin{matrix} 0 \\ 1 \end{matrix}$$

OR GATE

$$1. A + 0 = A$$

$$2. A + A = A$$

$$3. A + 1 = 1$$

$$4. A + \overline{A} = 1$$

$$A + 0$$

| Input | | Output |
|-------|---|--------|
| A | 0 | |
| 0 | 0 | 0 |
| 1 | 0 | 1 |

$$A + A$$

| Input | | Output |
|-------|---|--------|
| A | A | |
| 0 | 0 | 0 |
| 1 | 1 | 1 |

$$A + 1$$

| Input | | Output |
|-------|---|--------|
| A | 1 | |
| 0 | 1 | 1 |
| 1 | 1 | 1 |

$$A + \overline{A}$$

| Input | | Output |
|-------|----------------|--------|
| A | \overline{A} | |
| 0 | 1 | 1 |
| 1 | 0 | 1 |

BASIC RULES OF BOOLEAN ALGEBRA

AND GATE

$$1. A \cdot A = A$$

$$2. A \cdot 1 = A$$

$$3. A \cdot 0 = 0$$

$$4. A \cdot \bar{A} = 0$$

$$A \cdot A$$

| Input | | Output |
|-------|---|--------|
| A | A | |
| 0 | 0 | 0 |
| 1 | 1 | 1 |

$$A \cdot 1$$

| Input | | Output |
|-------|---|--------|
| A | 1 | |
| 0 | 1 | 0 |
| 1 | 1 | 1 |

$$A \cdot 0$$

| Input | | Output |
|-------|---|--------|
| A | 0 | |
| 0 | 0 | 0 |
| 1 | 0 | 0 |

$$A \cdot \bar{A}$$

| Input | | Output |
|-------|-----------|--------|
| A | \bar{A} | |
| 0 | 1 | 0 |
| 1 | 0 | 0 |

BASIC RULES OF BOOLEAN ALGEBRA

Rule 10

$$a) A + AB = A$$

$$b) \bar{A} + \bar{A}B = \bar{A}$$

AND-OR gate

$$\begin{aligned} a) A + AB &= A(1 + B) \\ &= A(1) \\ &= A \end{aligned}$$

$$\begin{aligned} b) \bar{A} + \bar{A}B &= \bar{A}(1 + B) \\ &= \bar{A}(1) \\ &= \bar{A} \end{aligned}$$

rule 2
rule 4

Rule 2

$$A + 1 = 1$$

↓

$$B + 1 = 1$$

Rule 4

$$A \cdot 1 = A$$

BASIC RULES OF BOOLEAN ALGEBRA

Rule 11

$$a) A + \bar{A}B = A + B$$

$$b) \bar{A} + AB = \bar{A} + B$$

OR-AND gate

$$\begin{aligned} a) A + \bar{A}B &= A + AB + \bar{A}B \\ &\downarrow \\ &A + AB \\ &= A + B(A + \bar{A}) \\ &= A + B(1) \\ &= A + B \quad \# \end{aligned}$$

$$\begin{aligned} b) \bar{A} + AB &= \bar{A} + \bar{A}B + AB \\ &\downarrow \\ &\bar{A} + \bar{A}B \\ &= \bar{A} + B(\bar{A} + A) \quad \text{rule 6} \\ &= \bar{A} + B(1) \quad \text{rule 4} \\ &= \bar{A} + B \quad \# \end{aligned}$$

Rule 10

$$A + AB = A$$

Rule 6

$$A + \bar{A} = 1$$

Rule 4

$$A(1) = A$$


$$B(1) = B$$

BASIC RULES OF BOOLEAN ALGEBRA

Rule 12

$$(A + B)(A + C) = A + BC$$

OR-AND gate

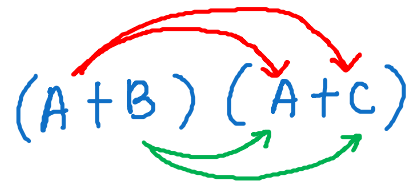
$$(A + B)(A + C)$$

rule 7

$$\begin{aligned} &= AA + AC + AB + BC \\ &= A + AC + AB + BC \\ &= A(1 + C + B) + BC \\ &= A(1) + BC \\ &= A + BC \quad \# \end{aligned}$$

Rule 7

$$A \cdot A = A$$

Rule 2

$$A + 1 = 1$$

$$C + B + 1 = 1$$

Rule 4

$$A \cdot 1 = A$$

BASIC RULES OF BOOLEAN ALGEBRA

AND & OR GATE

$$1. A + AB = A$$

$$2. A + \bar{A}B = A + B$$

$$\bar{A} + AB = \bar{A} + B$$

$$3. (A + B)(A + C) = A + BC$$

Rule 10

$$\begin{aligned} A + \bar{A}B &= A \\ \bar{A} + \bar{A}B &= \bar{A} \end{aligned}$$

Rule 11

$$\begin{aligned} A + \bar{A}B &= A + B \\ \bar{A} + AB &= \bar{A} + B \end{aligned}$$


Rule 12

$$(A + B)(A + C) = A + BC$$

DE MORGAN'S THEOREM


(NAND)
NOT AND
negative OR
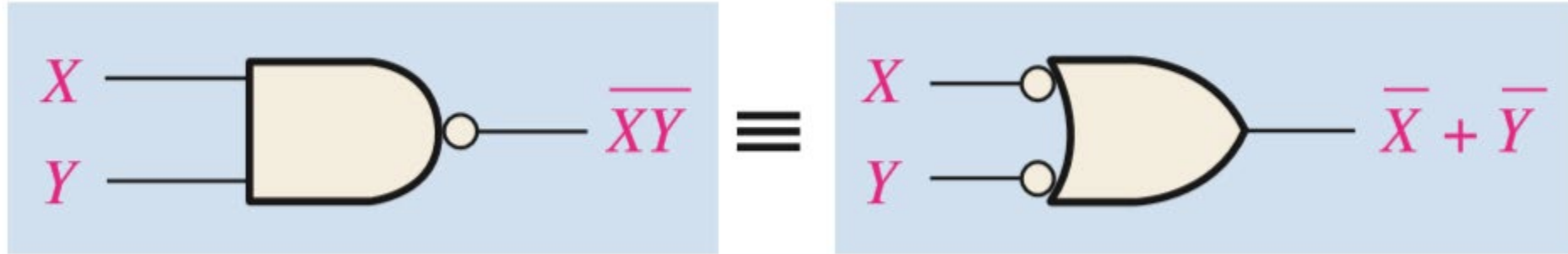
$$\overline{XY} = \overline{X} + \overline{Y}$$




(NOR)
NOT OR
negative AND
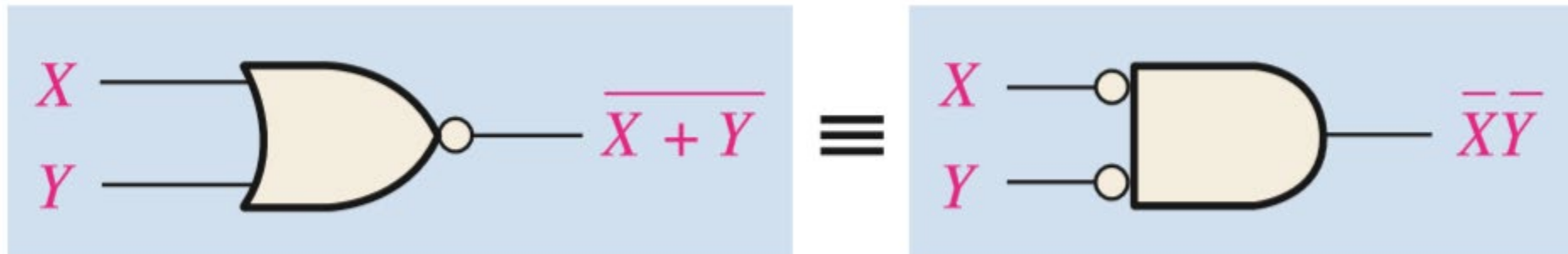
$$\overline{X + Y} = \overline{X} \overline{Y}$$




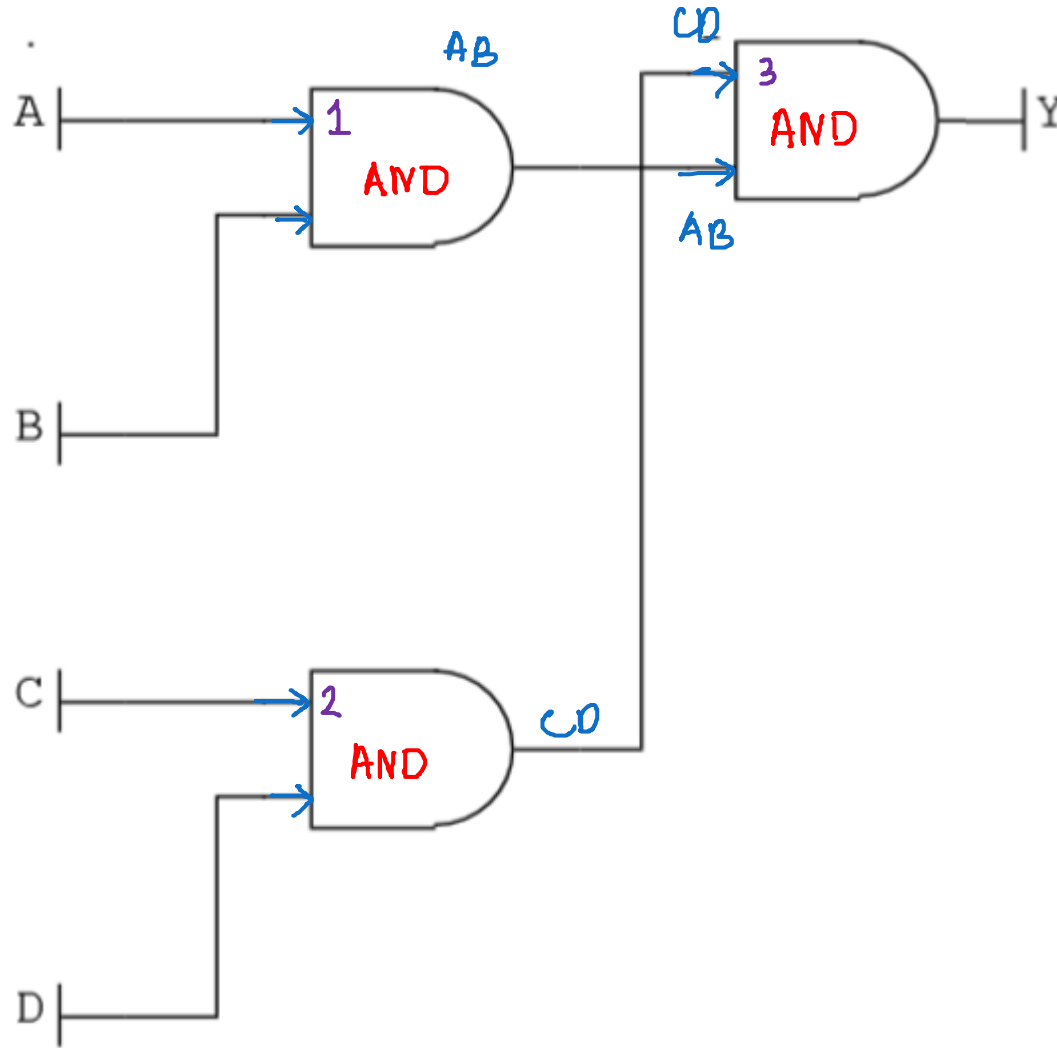Question 1(a) : Write the **BOOLEAN EXPRESSIONS** for the outputs from the following **logic circuits**



$$Y = AB \cdot CD$$
$$= ABCD \quad \#$$

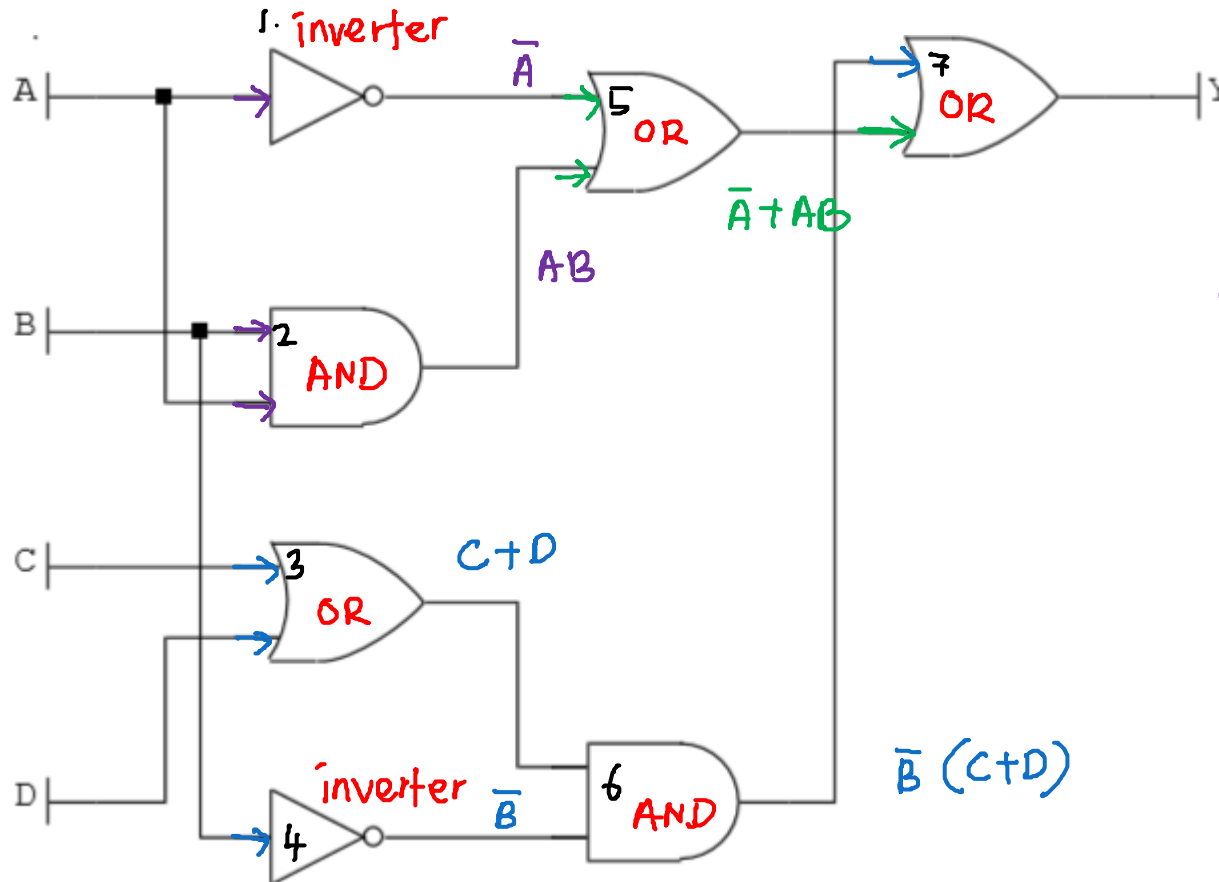Question 1(b) : Write the **BOOLEAN EXPRESSIONS** for the outputs from the following **logic circuits**



$$Y = (\bar{A} + AB) + [\bar{B}(C+D)]$$

Question 1(b) : Simplify **BOOLEAN EXPRESSIONS** from the following **logic circuits**

Method 1

$$Y = (\bar{A} + AB) + \bar{B}(C + D)$$

$$(\bar{A} + AB) + \bar{B}(C + D)$$

$$= \bar{A} + AB + \bar{B}C + \bar{B}D$$

$$= \bar{A} + \underline{B} + \bar{B}C + \bar{B}D$$

$$= \bar{A} + \underline{B+C} + \underline{\bar{B}D}$$

$$= \bar{A} + C + B + D$$

$$= \bar{A} + B + C + D \quad \text{✗}$$

rule 11

$$\bar{A} + AB = \bar{A} + B$$

$$A + \bar{A}B = A + B$$
$$\downarrow \quad \downarrow$$
$$B + \bar{B}C = B + C$$

$$B + \bar{B}D = B + D$$

Question 1(b) : Simplify **BOOLEAN EXPRESSIONS** from the following **logic circuits**

Method 2

$$Y = \bar{A} + AB + \bar{B}(C + D)$$

Example

$$\begin{array}{l} \bar{A} \cdot B \\ (\bar{A}) + (\bar{A}B) = A + B \\ \downarrow \quad \downarrow \\ (C) + (\bar{C}(AB + D)) = C + AB + D \\ \bar{C} \cdot (AB + D) \end{array}$$


$$\begin{aligned} & \underline{\bar{A} + AB + \bar{B}(C + D)} \\ &= \underline{\bar{A} + B} + \bar{B}(C + D) \\ &= \bar{A} + B + C + D \quad \# \end{aligned}$$

rule 11

$$\bar{A} + AB = \bar{A} + B$$

$$\begin{array}{l} A + \bar{A}B = A + B \\ \downarrow \quad \downarrow \quad \downarrow \\ B + \bar{B}(C + D) \\ \downarrow \quad \downarrow \\ = B + C + D \end{array}$$

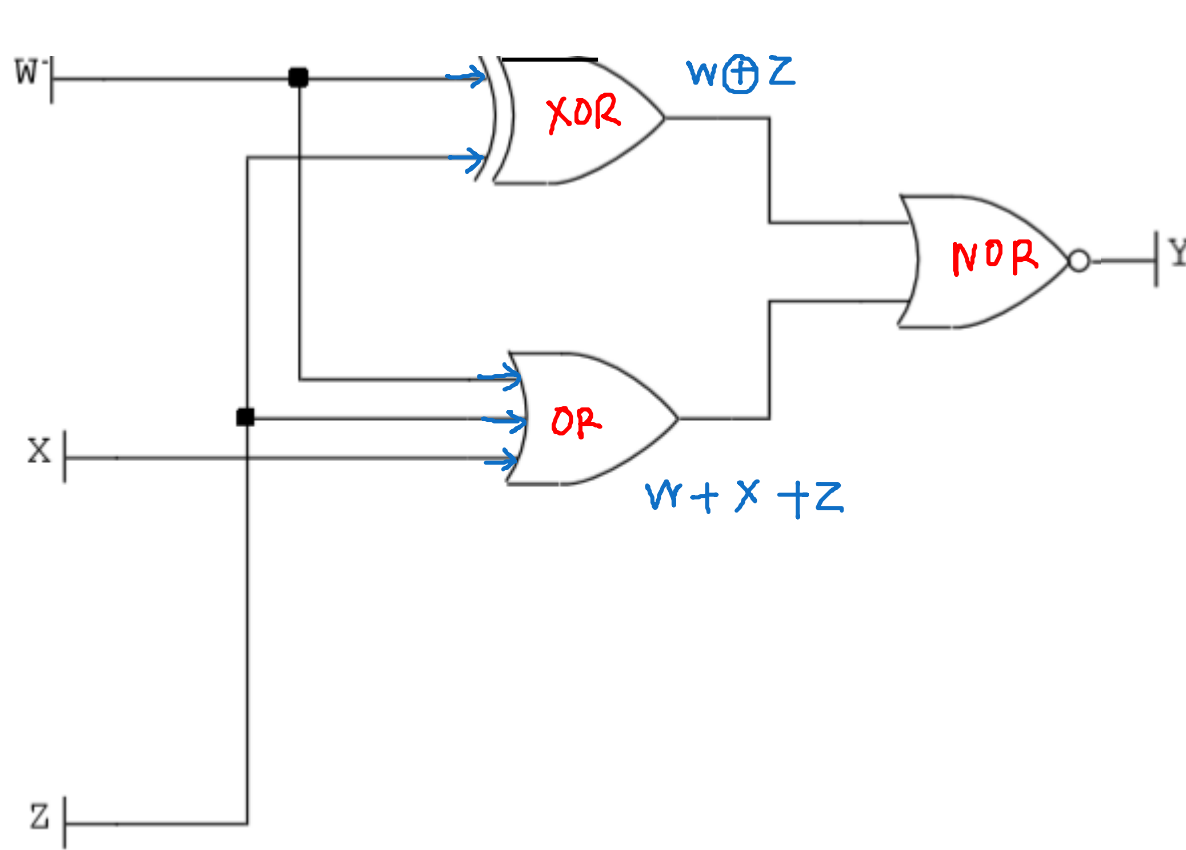Question 1(c) : Write the **BOOLEAN EXPRESSIONS** for the outputs from the following **logic circuits**



$$Y = \overline{(W \oplus Z) + (W + X + Z)}$$

not

OR

Question 1(c) : Simplify **BOOLEAN EXPRESSIONS** from the following **logic circuits**

ADDITIONAL

nor = negative and

$$Y = \overline{(W \oplus Z) + (W + X + Z)}$$

$$= \overline{(W \oplus Z)} \overline{(W + X + Z)} \quad \text{nor = negative AND}$$

$$\text{nor} \leftarrow = \overline{(W\bar{Z} + \bar{W}Z)} \overline{(W + X + Z)}$$

$$\text{NAND} \leftarrow = \overline{(W\bar{Z})} \overline{(\bar{W}Z)} \overline{(\bar{W}X\bar{Z})}$$

$$= \overline{(\bar{W} + \bar{Z})} \overline{(\bar{W} + \bar{Z})} \overline{(\bar{W}X\bar{Z})}$$

$$= \overline{(\bar{W} + Z)} \overline{(W + \bar{Z})} \overline{(\bar{W}X\bar{Z})}$$

$$= (\bar{W}\bar{W} + \bar{W}\bar{Z} + WZ + Z\bar{Z}) \overline{(\bar{W}X\bar{Z})}$$

$$\text{rule 7} \leftarrow = (\bar{W}\bar{Z} + WZ) \overline{(\bar{W}X\bar{Z})} \quad \text{rule 3}$$

$$= \bar{W}\bar{W}\bar{X}\bar{Z}\bar{Z} + \bar{W}\bar{W}\bar{X}Z\bar{Z}$$

$$= \bar{W}\bar{X}\bar{Z} + \bar{X}$$

$$= \bar{X}(\bar{W}\bar{Z} + 1) = \bar{X} \quad \text{X}$$

$$\text{rule 3} \\ A \cdot 0 = A$$

$$\text{rule 7} \\ A \cdot A = A$$

$$\text{rule 9} \\ \overline{\overline{A}} = A \\ \overline{\overline{Z}} = Z \\ \overline{\overline{W}} = W$$

$$\text{rule 8} \\ A \cdot \overline{A} = 0 \\ W \cdot \bar{W} = 0 \\ Z \cdot \bar{Z} = 0$$

$$\text{XOR} \\ W \oplus Z = W\bar{Z} + \bar{W}Z$$

$$\text{a) } \overline{W\bar{Z} + \bar{W}Z} = \overline{(W\bar{Z})} \overline{(\bar{W}Z)}$$


one term OR one term

$$\text{b) } \overline{(W\bar{Z})} \overline{(\bar{W}Z)} = \overline{(\bar{W} + \bar{Z})} \overline{(\bar{W} + \bar{Z})}$$

$$\text{c) } \overline{W + X + Z} = \overline{W} \overline{X} \overline{Z} \quad \text{nor negative AND}$$

$$\text{d) } (\bar{W} + Z)(\bar{W} + \bar{Z}) = W\bar{W} + \bar{W}\bar{Z} + WZ + Z\bar{Z}$$

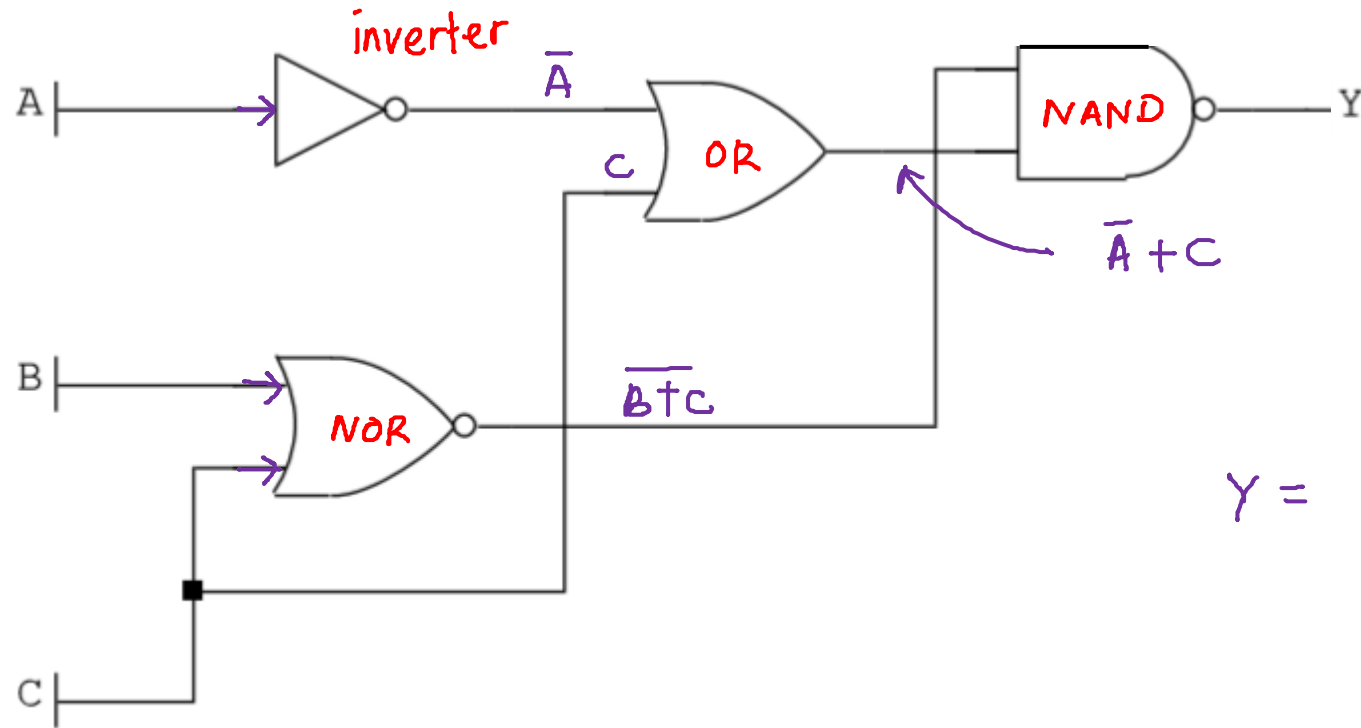Question 1(d) : Write the **BOOLEAN EXPRESSIONS** for the outputs from the following **logic circuits**



$$Y = (\bar{A} + C)(\overline{B+C})$$

Question 1(d) : Simplify **BOOLEAN EXPRESSIONS** from the following **logic circuits**

ADDITIONAL

NAND = negative OR

rule 9

$$\overline{\overline{A}} = A$$

$$\overline{\overline{B+C}} = B+C$$

$$Y = \overline{(\overline{A} + C)(\overline{B} + C)}$$

NOR $\leftarrow (\overline{A} + C) + (\overline{B} + C)$

$$= \overline{\overline{A}C} + B + C$$

$$= \overline{A}C + B + C$$

$$C + A + B$$

=


$$= A + B + C \quad \#$$

rule 11

$$\boxed{A} + \boxed{\overline{A}}B = A + B$$

$$\boxed{C} + \boxed{\overline{C}}A = C + A$$

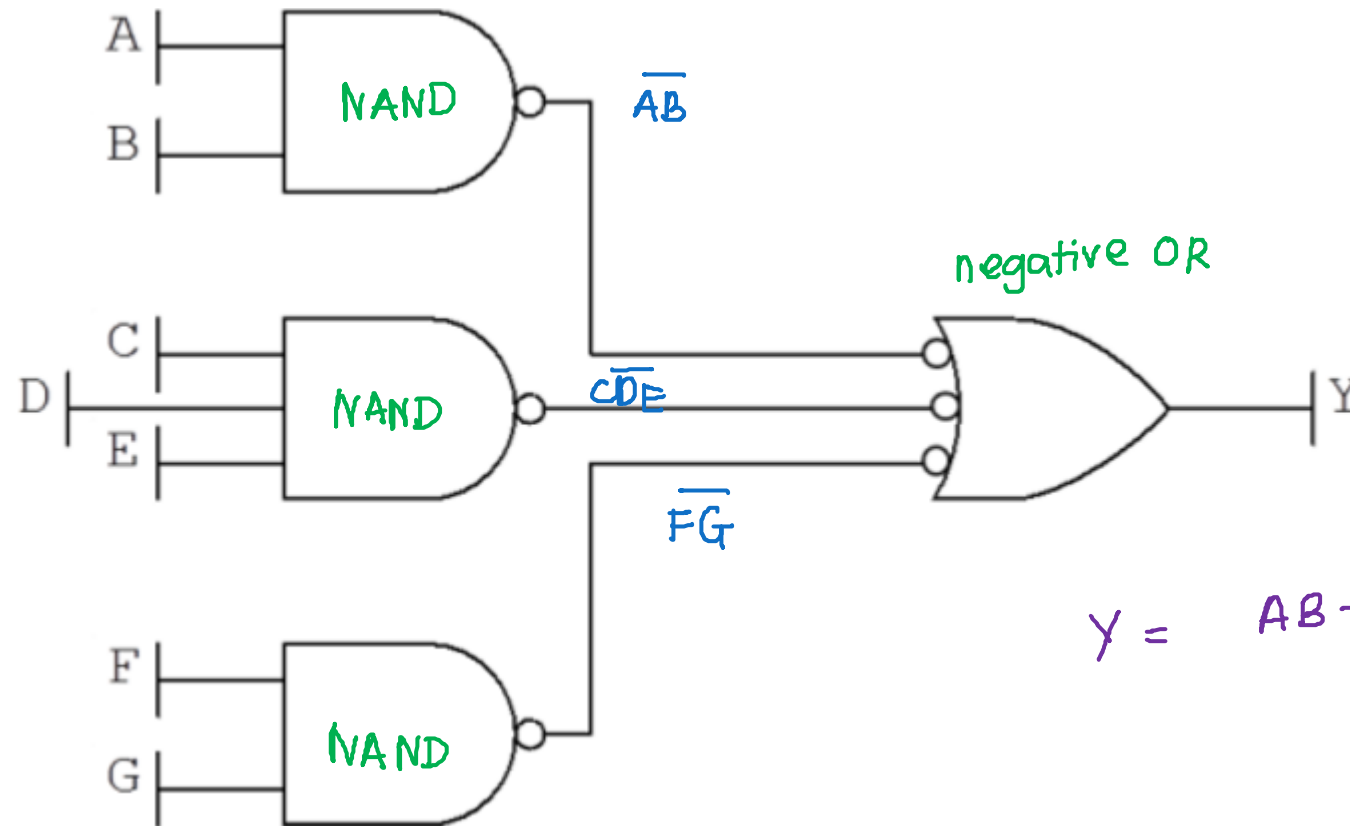Question 1(e) : Write the **BOOLEAN EXPRESSIONS** for the outputs from the following **logic circuits**



$$\begin{aligned}\overline{\overline{AB}} &= AB \\ \overline{\overline{CDE}} &= CDE \\ \overline{\overline{FG}} &= FG\end{aligned}$$

rule 9

$$\overline{\overline{A}} = A$$

$$Y = AB + CDE + FG \neq$$

END DISCUSSION PART 1
ANY QUESTIONS ??

