

LAB A-06 (Week 7) Construction and Implementation of Flip-flops, Counters, and Shift Registers

Objectives

- a. To get familiarity with the flip-flops, asynchronous counters, and shift registers by the construction of the circuit and studying the operation.
- b. To design and construct the synchronous counter and verify the counting sequence.

Tasks

1.
 - a. Verify the function table for 7476 Dual Negative Edge Triggered JK Flip-flop
 - b. Construct the following flip-flops using JK Flip-Flop and verify their truth tables
 - D (Data) Flip-Flop
 - T (Toggle) Flip-Flop
2. Design a 2-bit synchronous counter that can go through the following sequence in binary.

1, 3, 2, 0 and repeat

Use J-K Flip-flops for the design. Verify your design experimentally.
3. Construct and explain the operation of the following ripple counters with positive edge triggered D Flip-flops.
 - 4 bit binary asynchronous UP counter
 - 4 bit binary asynchronous DOWN counter
 - Asynchronous BCD Counter
 - Asynchronous MOD-12 Counter
 - Ripple divide by 14 Counter
4. Design and Construct a parallel counter that has the following sequence.
If the input (UP)/(DOWN)' = 1, it will count up, 000-010-100-110 and then recycle to 000
If the input (UP)/(DOWN)' = 0, it will count down, 110-100-010-000 and then recycle to 110.
Undesired states are don't care states.
 - (i) Use T flip-flops for the design.
 - (ii) Use D flip-flops for the design.

Report Format

Show all steps for each question and be self explanatory.


Assessment:

Total marks = 20/10=2%

Construction/Connections of the Circuit and Result during lab session= Tutor
to pick questions for students to do and submit via CircuitVerse = 10 marks,
Report =5 Questions \times 2 marks = 10 marks

Pin Configurations:

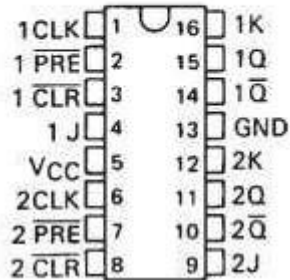SN5476, SN54LS76A . . . J PACKAGE
SN7476 . . . N PACKAGE
SN74LS76A . . . D OR N PACKAGE
(TOP VIEW)



'LS76A
FUNCTION TABLE

INPUTS					OUTPUTS	
PRE	CLR	CLK	J	K	Q	\bar{Q}
L	H	X	X	X	H	L
H	L	X	X	X	L	H
L	L	X	X	X	H [†]	H [†]
H	H	↓	L	L	Q ₀	\bar{Q}_0
H	H	↓	H	L	H	L
H	H	↓	L	H	L	H
H	H	↓	H	H	TOGGLE	
H	H	H	X	X	Q ₀	\bar{Q}_0

[†] This configuration is nonstable; that is, it will not persist when either preset or clear returns to its inactive (high) level.



TEXAS
INSTRUMENTS

POST OFFICE BOX 655303 • DALLAS, TEXAS 75265