

TUTORIAL 8

SEQUENTIAL LOGIC : FLIP FLOP


PDS0101: INTRODUCTION TO DIGITAL SYSTEMS
TRI 2, 2022-2023




Flip - Flop

S-R FF

PGT S-R FF


 


NGT S-R FF

 



JK FF

PGT JK FF

  

D FF



PGT D FF

  

Q start low / reset
reset

Q = 0

PGT SR FF
Q follow S
periodic

  

Truth table


$$2^2 = 4$$

SR Latch

| EN | S | R | Output | State |
|----|---|---|---------|---------|
| 1 | 0 | 0 | follow | rest |
| 1 | 0 | 1 | $Q = 0$ | reset |
| 1 | 1 | 0 | $Q = 1$ | set |
| 1 | 1 | 1 | follow | invalid |


0

EN = 1

 

PGT SR FF

| clk | S | R | Output | State |
|-----|---|---|---------|---------|
| ↑ | 0 | 0 | follow | rest |
| ↑ | 0 | 1 | $Q = 0$ | reset |
| ↑ | 1 | 0 | $Q = 1$ | set |
| ↑ | 1 | 1 | follow | invalid |

 

NGT SR FF

Q follow S
S R
0 1
1 0

| clk | S | R | output | state |
|-----|---|---|--------|---------|
| ↓ | 0 | 0 | follow | rest |
| ↓ | 0 | 1 | Q = 0 | reset |
| ↓ | 1 | 0 | Q = 1 | set |
| ↓ | 1 | 1 | follow | invalid |

NGT JK FF

Q follow J
J K
0 1
1 0

| clk | J | K | output | state |
|-----|---|---|--------|-----------|
| ↓ | 0 | 0 | follow | rest |
| ↓ | 0 | 1 | Q = 0 | reset |
| ↓ | 1 | 0 | Q = 1 | set |
| ↓ | 1 | 1 | toggle | set/reset |


PGT D FF Q follow D

| clk | D | | Output | state |
|-----|---|-----|--------|-------|
| ↑ | 0 | /// | Q = 0 | reset |
| ↑ | 1 | /// | Q = 1 | set |
| | | /// | | |
| | | /// | | |


Async
Sync

decade ; mod-12 counter
1010


| | | | |
|---|---|---|---|
| 8 | 4 | 2 | 1 |
| 1 | 0 | 1 | 0 |

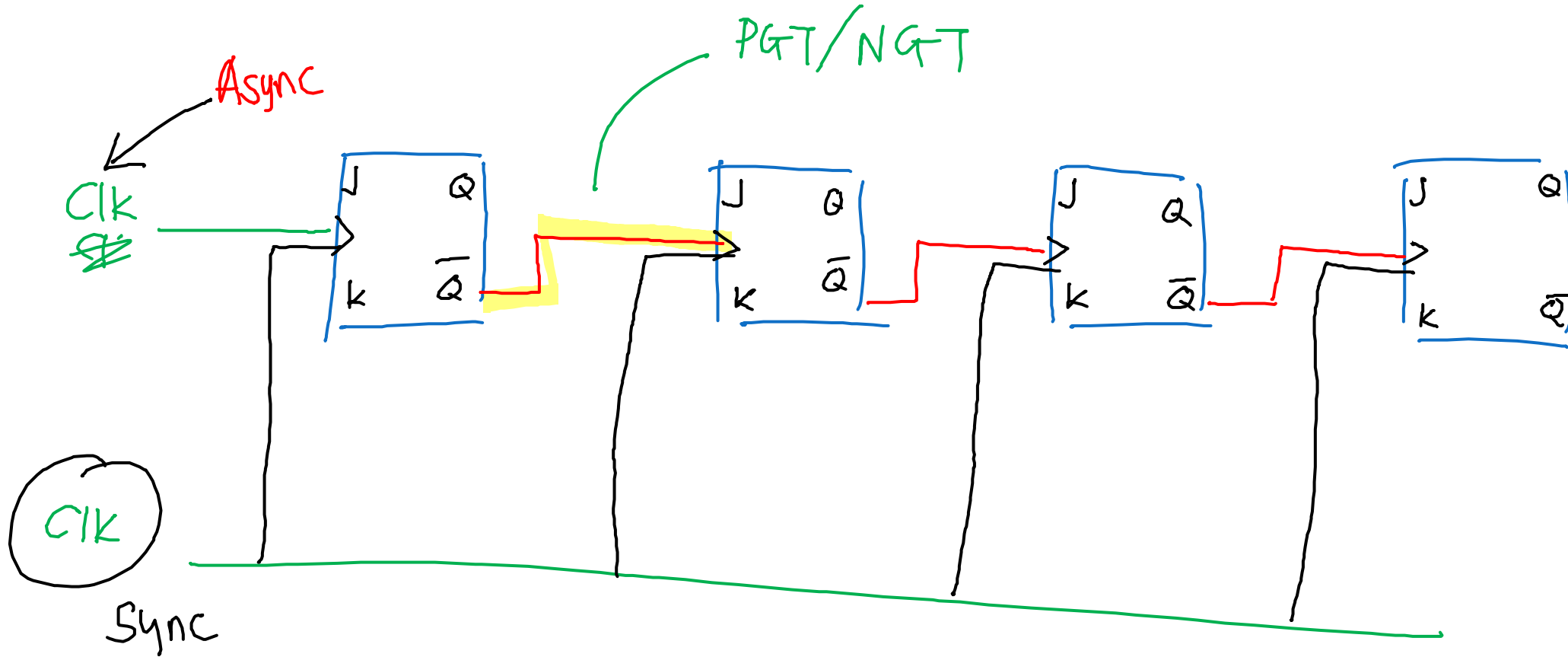

 1. Identify the two **flip-flops** shown below and draw their respective **timing diagrams** for their **Q** outputs based on the inputs shown. The FF are initially **RESET**. $Q = 0$




a) Negative Going Edge-triggered(NGT)

 


b) Positive Going Edge-triggered(PGT)


The FF are initially RESET. **Negative Going Edge-triggered(NGT)**

$Q = 0$

 


 The FF are initially RESET. **Positive Going Edge-triggered(PGT)**



 


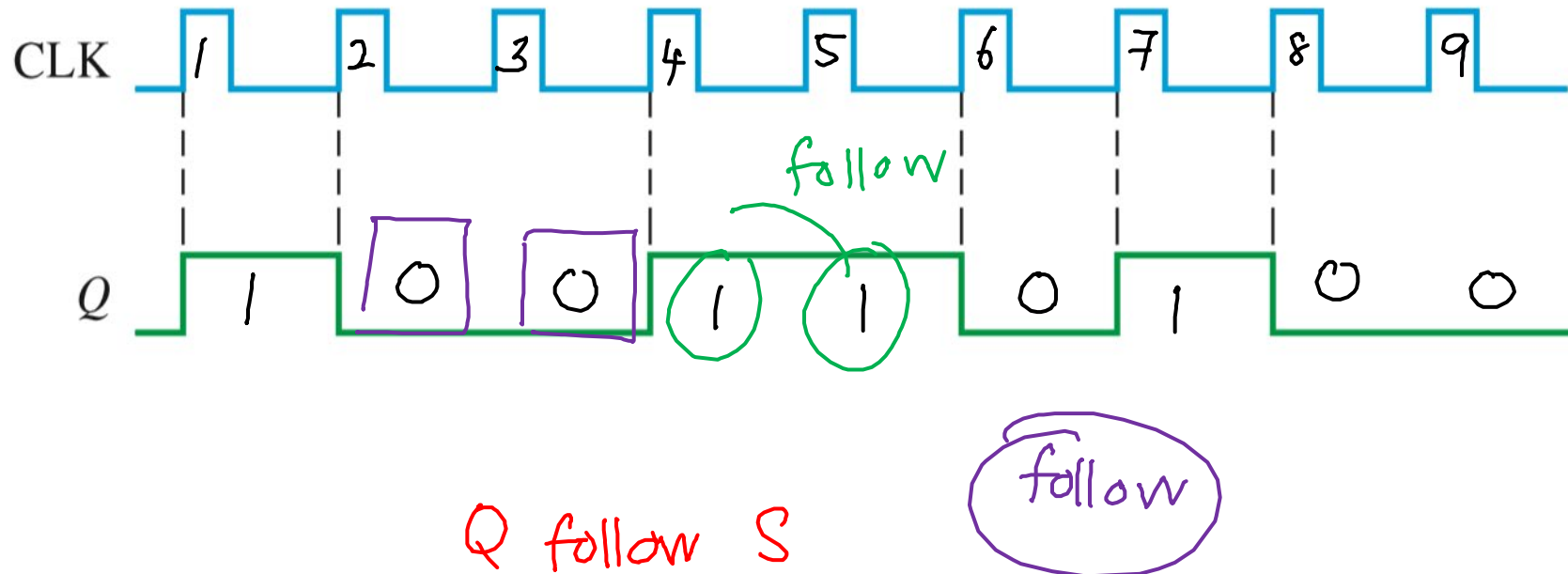2. The Q output of a **positive going ET** S-R flip-flop is shown in the timing diagram below. Determine the **correct inputs to S and R** that are required to produce this output.




| CLK | S | R | Q (OUTPUT) |
|-----|-------------|-------------|------------|
| 0 | | | |
| 1 | 1 | 0 | 1 |
| 2 | 0 | 1 | 0 |
| 3 | 0 0 1 | 1 0 1 | 0 |
| 4 | 1 | 0 | 1 |
| 5 | 0 1 1 | 0 0 1 | 1 |
| 6 | 0 | 1 | 0 |
| 7 | 1 | 0 | 1 |
| 8 | 0 | 1 | 0 |
| 9 | 0 0 1 | 0 1 1 | 0 |

 
2. The Q output of a **positive going ET** S-R flip-flop is shown in the timing diagram below. Determine the **correct inputs to S and R** that are required to produce the this output.



 
3. Draw the Q output of a **D flip-flop** with the inputs shown in the timing diagram below. You may assume that the FF is positive going triggered and **Q** is initially **LOW** $Q = 0$



 4. For a **positive** going ET J-K flip-flop with inputs as shown below, determine the Q output relative to the CLK if Q starts out **LOW**





 5. For a **positive** going ET J-K flip-flop with inputs as shown below, determine the Q output relative to the CLK if Q starts out **LOW**




6. For the circuit shown below, determine the output of **Q** (which starts out **LOW**) based on the inputs shown the in the timing diagram

All input ONE; output ONE

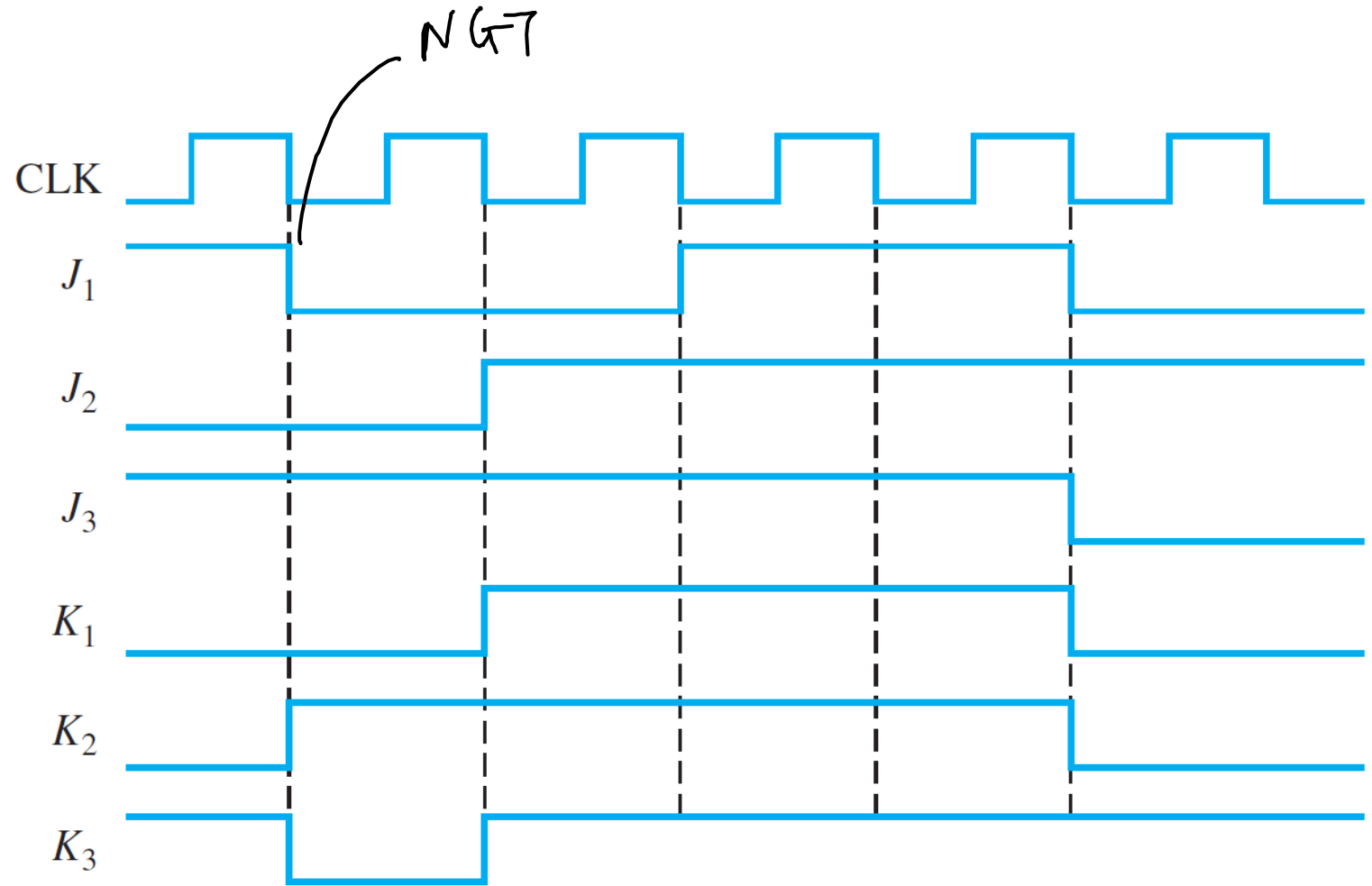 


6. For the circuit shown below, determine the output of **Q** (which starts out **LOW**) based on the inputs shown in the timing diagram


$Q_0 = 0$ ↙

 

| CLK | J ₁ | J ₂ | J ₃ | J | K ₁ | K ₂ | K ₃ | K | Q |
|-----|----------------|----------------|----------------|---|----------------|----------------|----------------|---|---|
| 1 | 1 | 0 | 1 | 0 | 0 | 0 | 1 | 0 | 0 |
| 2 | 0 | 0 | 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| 3 | 0 | 1 | 1 | 0 | 1 | 1 | 1 | 1 | 0 |
| 4 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |
| 5 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 0 |
| 6 | 0 | 1 | 0 | 0 | 0 | 0 | 1 | 0 | 0 |

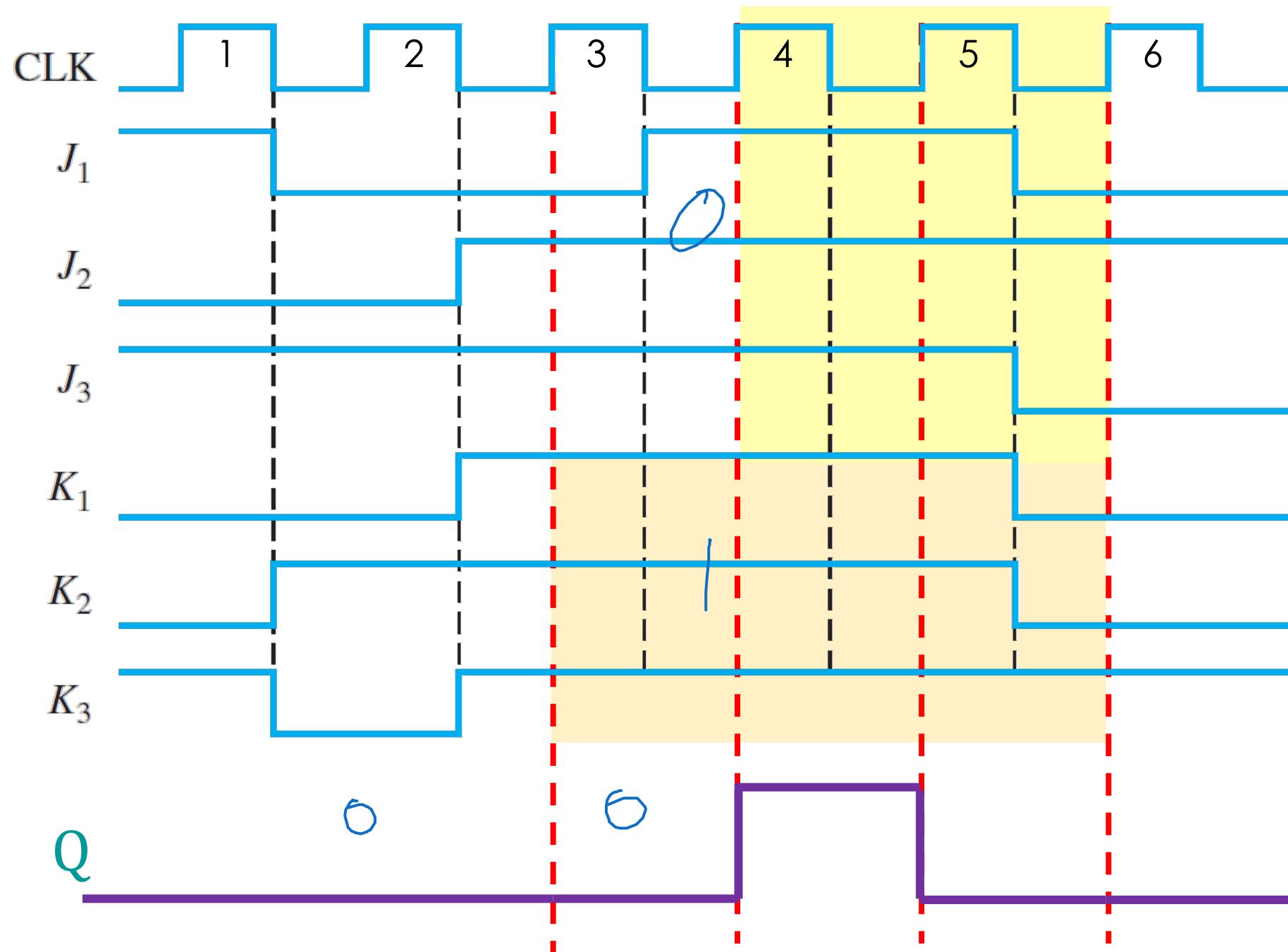

 7. For a **negative** going ET J-K FF with the inputs shown below, determine the Q output waveform relative to the CLK if **Q is initially RESET** $Q = 0$



**END DISCUSSIONS
ANY QUESTIONS ??**

