

Objectives

- To design and implement a priority **encoder** circuit.
- To design and implement the higher order **decoder** using lower order decoder ICs.
- To design a given arithmetic circuit
- To design the combinational logic circuit with the given Boolean expression using a suitable **MUX**/ decoder
- To design the given **code converter** circuits.

Tasks

- Design a **3 input priority encoder circuit**. The inputs are $a_3a_2a_1$, with a_3 having the lowest priority and a_1 the highest. The outputs are y_2y_1 , indicating the encoded highest-priority active input, and v , the valid output which indicates that at least one input is active. (Note: **Priority input a_3** is encoded as **11**, **a_2** as **10** and **a_1** as **01**)

Perform the following:

- Construct the truth table
- Simplify the Boolean expressions for y_2, y_1 , and v using Karnaugh map techniques.
- Draw the logic diagram with necessary basic logic gates.
- Verify your design experimentally

- Design and construct a **3 to 8 decoder circuit using 2-line-to-4-line decoder** and also other logic gates needed.

Perform the following:

- Form the truth table for higher order decoder (3 to 8 decoder)
- Design higher order decoder using the given lower order decoder.
- Draw the logic diagram for higher order decoder using two lower order decoders
- Verify the truth table of 3 to 8 decoder (higher order decoder) by implementing the logic diagram with lower order decoder (2 to 4 decoder) and other necessary logic gate(s).

- Design a **full subtractor circuit** using
 - Two half subtractors.
 - Using only NAND gates
 - Using Only NOR gates.

- Implement the following Boolean expression

$$F(W, X, Y, Z) = \sum m(1, 2, 4, 6, 7, 9, 11, 14, 15)$$

- Using **8x1 MUX** and the needed logic gates
- Using **16x1 MUX** and the needed logic gates.
- Using a suitable decoder and an OR gate.

- Design code converter circuits for the following problems:

- 3-bit Gray-to- binary code converter
- 3-bit Binary-to-Gray code converter
- (8 4 -2 -1) BCD code to (Excess 3) BCD code converter

For the above design problems

- Construct the truth table
- Simplify the Boolean expressions using K-map/Boolean Algebra techniques
- Draw the logic diagram

Report Format


- Objectives
- Question 1 to 5
 - Problem Statement
 - Answer by following the subdivisions given in each question
- Conclusion

Assessment:

Total marks = 20/10=2%

Construction/Connections of the Circuit and Result during lab session = Tutor to pick questions for students to do and submit via CircuitVerse = 10 marks,

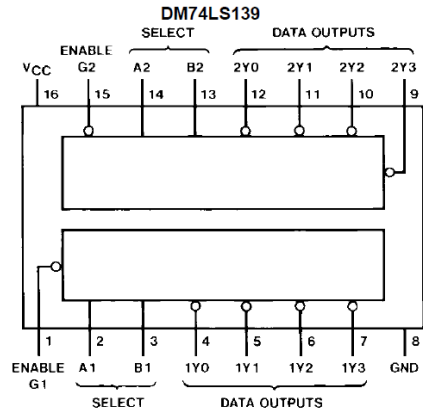Report = 5 Questions × 2 marks = 10 marks



DM74LS139

Inputs			Outputs			
Enable	Select					
G	B	A	Y0	Y1	Y2	Y3
H	X	X	H	H	H	H
L	L	L	L	H	H	H
L	L	H	H	L	H	H
L	H	L	H	H	L	H
L	H	H	H	H	H	L

H = HIGH Level
L = LOW Level
X = Don't Care

Note 1: $G2 = G2A + G2B$

